

Circuit Bending:

1. Nothing

Always reading High because the closest is source.

2. Always Low

Goes to ground so the digital read will be 0V (LOW)

3. Button now turns on led

Closest is 5V when the switch(button) is on so it will read 5V instead of ground. Pull up circuit.